Nama: Banu Wisnu Murti

NIM : L200180133


Percobaan 1

CD	00	01	11	10
00	0	0	0	0
01	1	1	1	0
11	0	1	1	1
10	0	0	0	0

Fungsi boolean sederhana:

$$F = BD + A'C'D + ACD$$

Gambar:

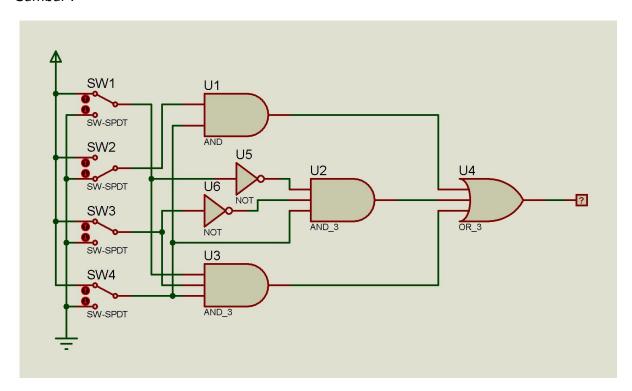


CD	00	01	11	10
00	1	0	0	1
01	0	1	1	0
11	0	1	1	0
10	1	0	0	1


Fungsi Boolean sederhana :

$$F = BD + B'D'$$
 (AND-OR)

$$F = (B + D')(B' + D) \qquad (OR-AND)$$

Gambar:

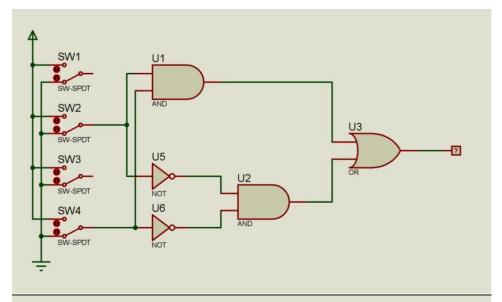

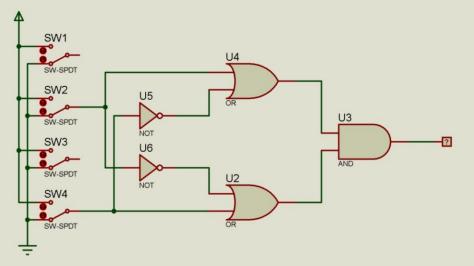


Fungsi Boolean : F = XYZ + XYZ' + XY'Z + X'YZ + X'YZ' + XY'Z' + XY'Z'

z XY	00	01	11	10
0	1	1	1	1
1	0	1	1	1

Fungsi Boolean sederhana:

$$F = C' + B + A$$

Gambar :

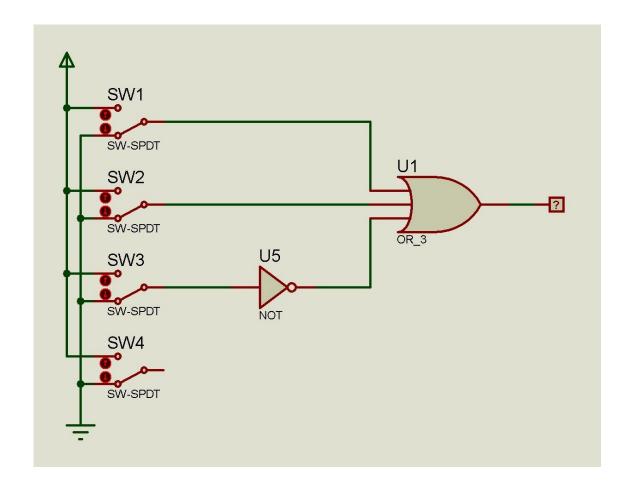


Fungsi Boolean : F = AD' + ABC + ABC' + BCD + BC'D' + AB'CD'

CD	00	01	11	10
00	0	1	1	1
01	0	0	1	0
11	0	1	1	0
10	0	0	1	1

Fungsi Boolean sederhana:

$$F = AB + AD' + BCD + BC'D'$$


Gambar:

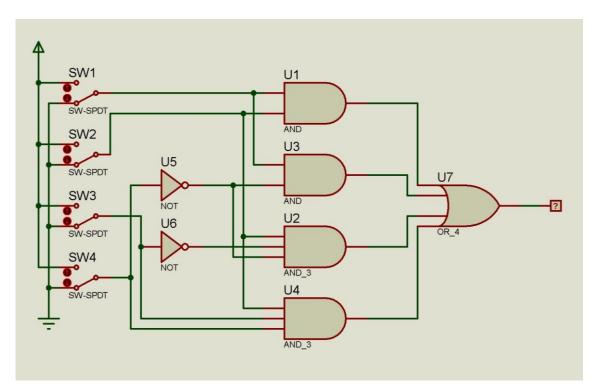

CD	00	01	11	10
00	1	0	1	0
01	1	0	1	1
11	1	1	0	0
10	1	0	0	1

Fungsi Boolean sederhana:
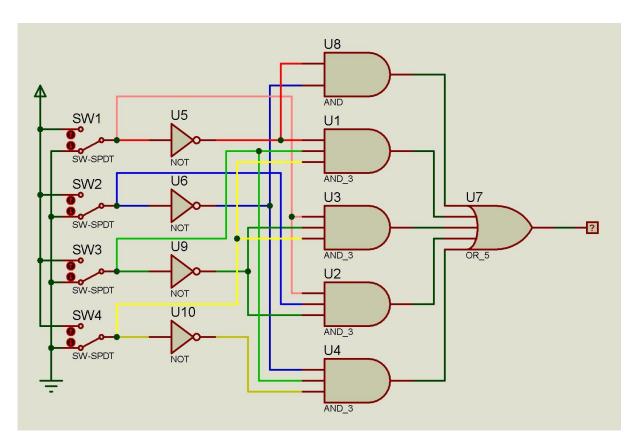
$$F = A'B' + A'CD + AC'D + ABC' + B'CD'$$
 Gambar:



Apakah kedua kombinasi memberikan hasil yang sama? Ya / Tidak